 


# Timing and Advanced Adders

## 1 Timing

- A buffer doesn't change if an output is high or low, it just makes it either full high or full low


In any physical gate or circuit there is a delay between the input changing and the output adjusting appropriately.



- Note that the lines are not vertical, they rise between low and high

**Propagation delay:**  $t_{pd}$ : The max delay before the output is stable

 **Contamination delay:**  $t_{cd}$ : The min delay before the output changes




Delay is caused by:

- Capacitance and resistance in a circuit
- Speed of light limitation

Reasons why  $t_{pd}$  and  $t_{cd}$  may be different:

- Different rising and falling delays
- A circuit may have multiple inputs and outputs, some of which are faster than others
- Circuits slow down when hot and speed up when cold

## 2 Critical paths

 

In a circuit the critical path is the path determining the propagation delay of the circuit - i.e. the longest path in the circuit


$$t_{pd} = 2t_{pd\_AND} + t_{pd\_OR}$$

The short path is the path determining the contamination delay of the circuit - i.e. the shortest path in the circuit

$$t_{cd} = t_{cd\_AND}$$
 
### 3 Glitches

Sometimes the output can temporarily move to an incorrect value before stabilising. This is called a glitch.




With  $a=0, b=1$  and  $c=1$ . If  $b$  falls to 0, the output will change from 1 to 0 to 1.

### 4 Mux delays

4-line multiplexor circuits.

Different characteristics for **selector change** and **data change**


Gate	$t_{pd}$ (ps)
<b>NOT</b>	<b>30</b>
AND	60
<b>3-AND</b>	<b>80</b>
4-OR	90
<b>Tristate (D)</b>	<b>50</b>
Tristate (S)	35

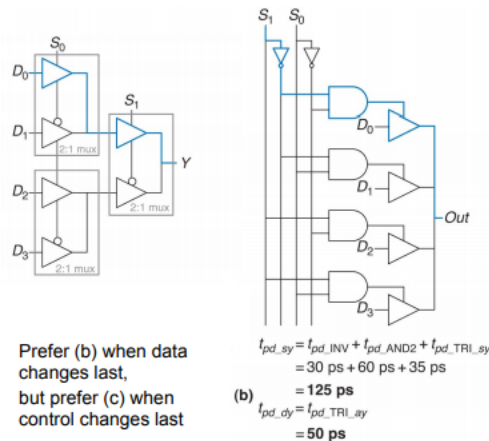

- Tristate D - Data
- Tristate S - Selector
- The different speeds for different changes need to be taken into account for whatever the use is
 
### 5 Adder

The full adder circuit we have looked at takes **3 gate delays** for the carry out to be computed:




**Time 0** **Time 1** **Time 2** **Time 3**

If we can **pre-compute the first level**, there are only 2 gate delays once the carry in arrives.

N.B. I am counting all gates as 1 time step. In reality some take longer than others.
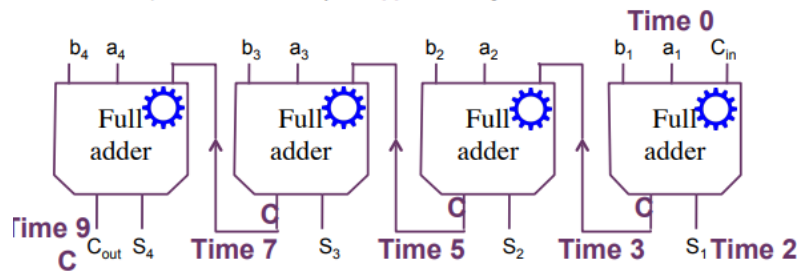
## 6 Ripple adder

The computation of the carry bit **ripples** through the chained adders:




A k-bit ripple adder will take  $3+2(k-1)=2k+1$  gate delays to compute  $C_{out}$ .  
So a 32-bit adder takes 65 gate delays!

- 3 time steps for 1st carry, then 2 time steps for each after that as the first level is pre computed

## 7 Faster Adders - idea

8-bit ripple adder takes 17 gate delays.

 

**Key idea:** for later bits pre-compute the outcome with both carry in and no carry in, then quickly select the right answer.

Faster addition at the expense of more circuitry.

- This uses  $c_4$  for the multiplexor and makes large additions much faster, at the expense of more circuitry

## 8 Carry-Lookahead Adder

The 8 rules of binary addition:

$$\begin{array}{ll} 0 + 0 = 0 & C_{in} + 0 + 0 = 1 \\ 0 + 1 = 1 & C_{in} + 0 + 1 = 0 \text{ with } C_{out} \\ 1 + 0 = 1 & C_{in} + 1 + 0 = 0 \text{ with } C_{out} \\ 1 + 1 = 0 \text{ with } C_{out} & C_{in} + 1 + 1 = 1 \text{ with } C_{out} \end{array}$$

Define two functions.

**Generate:**  $G(A,B) = 1$  if A and B would cause  $C_{out}$  even if  $C_{in} = 0$ .


**Propagate:**  $P(A,B) = 1$  if A and B would cause  $C_{out}$  if  $C_{in} = 1$ .

$$G(A,B) = A \text{ AND } B$$

$$P(A,B) = A \text{ OR } B$$

Carry occurs if it is either **generated** or there is carry in and it is **propagated**:
 
$$C_{out} = G(A,B) + P(A,B) \cdot C_{in}$$




$$C_{out} = G_4 + P_4G_3 + P_4P_3G_2 + P_4P_3P_2G_1 + P_4P_3P_2P_1 \cdot C_{in}$$


We can compute every  $P_i$  and  $G_i$  in one gate delay

So we can compute  $C_{out}$  (and all the intermediate carries) in 3 gate delays (1 for  $P_i, G_i$ , an AND layer and an OR layer).

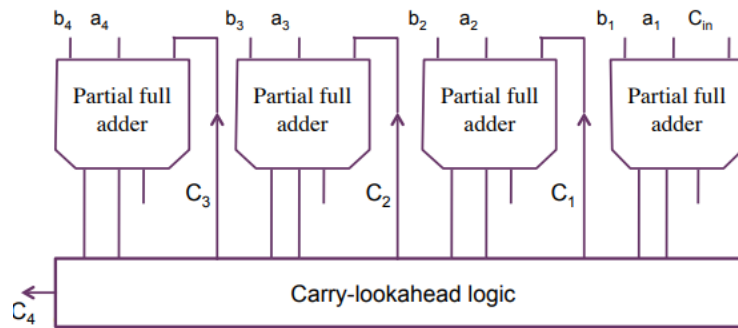We could compute the full sum in 4 gate delays!




## 9 Partial Full Adder

 

## 10 MSI Chip


### MSI chip 74x283

4-bit CLA adder

 

Notes:

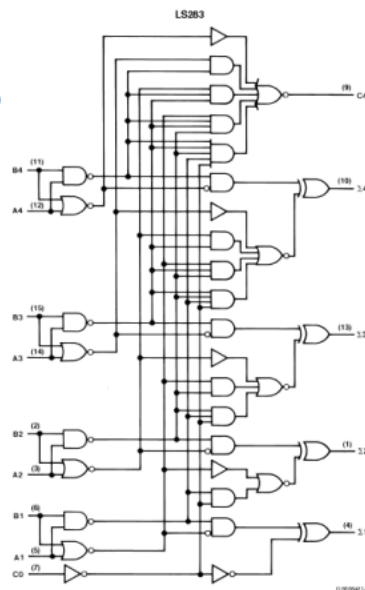
- Gate depth 4
- Requires gates with many inputs



## 11 More on the carry-lookahead adder


We could create a CLA which adds  $n$ -bit numbers in constant gate delay. It would require order  $n^2$  gates and gates taking order  $n$  inputs. This is impractical for large  $n$ .

**First solution:** chain 4-bit CLAs

 

The carry now ripples along the chain 4-times as fast as originally

## 12 2 Level Carry-Lookahead Adder

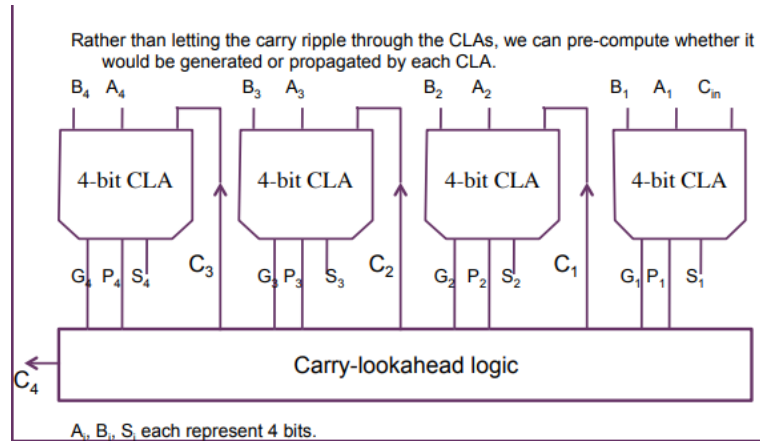

We now have a 16-bit 2-level CLA.

**Gate delays:**

- 1 gate delay to compute first level  $G_s$ ,  $P_s$
- 2 gate delays to compute second level  $G_s$ ,  $P_s$
- 2 gate delays to compute carries
- 1 gate delay to compute sums

**Total 6 gate delays.**

A standard 16-bit ripple carry adder would take 33 gate delays.


These 16-bit adders could be chained to give an  $n$ -bit adder with gate delay  $2(n/16)+4$ .

Alternatively, a 3 (or more) level CLA could be used to create an  $n$ -bit adder with delay  $O(\log n)$  and not too much circuitry.

## 13 Example

A	0 1 1 0 1 1 1 0 1 0 1 0	: 1770
B	+0 0 1 1 0 1 0 1 0 1 1 0	: 854
Sum	1 0 1 0 0 1 0 0 0 0 0 0	: 2624

Input bits (A,B) Output bits (G,P,S)

 

## 14 Summary

- $t_{pd}$  - propagation delay (time until last answer comes in)
- $t_{cd}$  - contamination delay (time before any change)
- $t_{pcq}$  - max time until recorded after tick
- $t_{ccq}$  - How long before the value is recorded after the tick
- $t_{setup}$  - time stable at least this long before tick
- $t_{hold}$  - time stable at least this long after tick

## 15 Improving clock speed

- Putting registers in allows you to reduce the long delays, allowing a faster clock speed
- Work like a production line by separating the jobs
- Allows 1st half to work on next calculation while 2nd half is working on the end of the calculation
- First half takes less time than all of previous one, allowing for a faster clock speed
- So overall a calculation takes 2 clock ticks, so the latency will be larger, but the time for a large number of calculations will reduce drastically
- If you keep adding registers it keeps getting better, but the resources required mean that you get diminishing returns